

Solution

CET25P7 ALTERNATING CURRENT

Class 12 - Physics

1.
(c) Pure resistive circuit
Explanation: Since in pure resistive circuit the current and voltage are in phase, the power dissipation is maximum.
2.
(d) $L/2$
Explanation: The resonance frequency is given by
$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
When C is changed to $2C$, f_0 will remain unchanged, if L is changed to $L/2$.
3.
(d) 300 volt
Explanation: 300 volt
4.
(c) 161 V
Explanation: $R = 300.0 \Omega$, $X_C = 300.0 \Omega$ and $X_L = 500.0 \Omega$, $P_{av} = 60W$
$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{300^2 + (500 - 300)^2} = 100\sqrt{13}\Omega$$
$$P_{av} = V_{rms} \times I_{rms} \times \cos \phi$$
Now, $I_{rms} = \frac{V_{rms}}{Z}$
$$\cos \phi = \frac{R}{Z}$$
Thus, $P_{av} = \frac{(V_{rms})^2}{Z} \times \frac{R}{Z} = \frac{(V_{rms})^2 R}{Z^2}$
$$60 = \frac{(V_{rms})^2 \times 300}{100\sqrt{13} \times 100\sqrt{13}}$$
$$V_{rms} = \sqrt{\frac{60 \times 100 \times 13}{3}} = 161V$$
5.
(d) 0 V
Explanation: Average value of AC voltage for a half cycle is positive and similarly, the mean value of AC voltage for other half cycle is negative.
Average potential difference between the two terminals for complete full cycle,
$$V_{av} = (0.637V_0) + (-0.637V_0) = 0 \text{ V}$$
6.
(c) 120 V
Explanation: Flux linked with the primary coil,
$$\phi = \phi_0 + 4t$$
Voltage across primary,
$$V_p = \frac{d\phi}{dt} = 0 + 4 \times 1 = 4 \text{ V}$$
Voltage across secondary,
$$V_s = \frac{N_s}{N_p} \cdot V_p = \frac{1500}{50} \times 4 = 120 \text{ V}$$
7.
(d) zero
Explanation: Since reactive impedance at resonance is zero and we know that,
$$\tan \phi = X_L - \frac{X_C}{Z}$$
but $X_L - X_C = 0$
therefore $\phi = 0$

8.

(d) $22 \times 10^3 \text{ cal}$

Explanation: $H = \frac{\varepsilon_{rms}^2 t}{RJ} = \frac{\varepsilon_0^2 t}{2RJ} = \frac{(220)^2 \times 7 \times 60}{2 \times 110 \times 4.2}$
 $= 22 \times 10^3 \text{ cal}$

9. (a) 0.239 H

Explanation: $X_L = 120\Omega$, $f = 80\text{Hz}$

Now,

$$X_L = \omega L = 2\pi f L$$

$$L = \frac{X_L}{2\pi f} = \frac{120}{2 \times 3.14 \times 80} = 0.239 \text{ H}$$

10.

(d) 198 V

Explanation: $V_{av} = \frac{2}{\pi} V_0 = \frac{2}{\pi} \times (V_{rms} \times \sqrt{2}) = \frac{2\sqrt{2}}{\pi} \cdot V_{rms}$
 $= \frac{2\sqrt{2}}{\pi} \times 220 = 198 \text{ V}$

11.

(b) $3.2 \times 10^{-3} \text{ A}$, 0.16 A

Explanation: $\frac{I_1}{I_2} = \frac{3.2 \times 10^{-3}}{0.16} = \frac{1}{50} = \frac{10}{500} = \frac{N_2}{N_1}$

12.

(c) 10 W

Explanation: Let P = actual power used

W = power specified = 40 W

V_A = Applied voltage = 100 V

V_S = Specified voltage = 200 V

Now,

$$P = \left(\frac{V_A}{V_S} \right)^2 W$$

$$P = \left(\frac{100}{200} \right)^2 \times 40 = 10 \text{ W}$$

13. (a) 4800 W, 0.6

Explanation: $R = 3\Omega$

$L = 25.48 \text{ mH}$

$C = 796 \mu\text{F}$

$V_{rms} = 283 \text{ V}$

$f = 50 \text{ Hz}$

Impedance

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 25.48 \times 10^{-3} = 8\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 796 \times 10^{-6}} = 4\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{3^2 + (8 - 4)^2} = 5\Omega$$

Power dissipated in the circuit,

$$P = i^2 R$$

$$i = \frac{i_m}{\sqrt{2}} = \frac{1}{\sqrt{2}} \frac{V_{rms}}{Z} = \frac{1}{\sqrt{2}} \times \frac{283}{5} = 40 \text{ A}$$

$$P = i^2 R = 40 \times 40 \times 3 = 4800 \text{ W}$$

power factor,

$$\cos \phi = \frac{R}{Z} = \frac{3}{5} = 0.6$$

14. (a) soft iron

Explanation: Soft iron provides the best material for the core of a transformer as its permeability (μ) is very high. Its hysteresis curve is of small area and its coercivity is very low.

15. (a) 3 V

Explanation: $\varepsilon_2 = \frac{N_2}{N_1} \cdot \varepsilon_1 = \frac{2}{1} \times 1.5 = 3 \text{ V}$

16. (a) $\frac{15}{\sqrt{2}}$ A

Explanation: $I = I_0 \sin \omega t$

$$I = I_{\text{rms}} \times \sqrt{2} \times \sin(2\pi ft)$$

$$\text{or, } I = 15 \times \sqrt{2} \times \sin \frac{2 \times \pi \times 50}{600}$$

$$\text{or, } I = 15 \times \sqrt{2} \times \sin \left(\frac{\pi}{6} \right)$$

$$I = \frac{15}{\sqrt{2}} \text{ A}$$

17. (a) 66 V, 210 V

Explanation: $R = 100 \Omega$

$$C = 10 \mu F$$

$$V = 220 \text{ volt}$$

$$f = 50 \text{ Hz}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.14 \times 50 \times 10 \times 10^{-6}} = 318.5 \Omega$$

$$Z = \sqrt{(100)^2 + (318.5)^2} = 333.8 \Omega$$

Current in circuit,

$$i = \frac{V}{Z} = \frac{220}{333.8} = 0.66 \text{ A}$$

$$\text{Voltage across the resistor, } V_R = iR = 0.66 \times 100 = 66 \text{ V}$$

$$\text{Voltage across the capacitor, } V_C = iX_C = 0.66 \times 318.5 = 210 \text{ V}$$

18.

(c) $\frac{1}{400}$ s

Explanation: $I = I_0 \sin 2\pi ft = 100 \sin 200\pi t$

$$\therefore 2f = 200 \text{ or } f = 100 \text{ Hz}$$

$$T = \frac{1}{f} = \frac{1}{100} \text{ s}$$

Time taken by current to rise from zero to peak value

$$= \frac{T}{4} = \frac{1}{4 \times 100} \text{ s} = \frac{1}{400} \text{ s}$$

19.

(c) 1.06 A

Explanation: Maximum value of current, $i_0 = 1.5 \text{ A}$

Thus, root-mean-square current,

$$i_{\text{rms}} = \frac{i_0}{\sqrt{2}} = \frac{1.50}{\sqrt{2}} = 1.06 \text{ A}$$

20. (a) 0.8

Explanation: Power factor $\cos \phi = \frac{R}{Z}$

Here, $R = 12 \text{ ohm}$ and $Z = 15 \text{ ohm}$

$$\therefore \text{power factor} = \frac{12}{15} = 0.8$$

21.

(b) $7.54 \times 10^2 \text{ m}$

Explanation: Resonant frequency,

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{8 \times 10^{-6} \times 0.02 \times 10^{-6}}} \text{ Hz}$$

$$= 3.98 \times 10^5 \text{ Hz}$$

Resonant wavelength,

$$\lambda = \frac{c}{f_r} = \frac{3 \times 10^8}{3.9 \times 10^5}$$

$$= 7.54 \times 10^2 \text{ m}$$

22. (a) 600Ω , 200Ω and 500Ω

Explanation: Given that

$$R = 300 \Omega$$

$$L = 60 \text{ mH} = 60 \times 10^{-3} \text{ H}$$

$$C = 0.5 \mu F = 0.5 \times 10^{-6} F$$

$$V = 50 \text{ volt}$$

$$\omega = 10000 \text{ rad/s}$$

$$\text{Inductive reactance, } X_L = \omega L = 10000 \times 60 \times 10^{-3} = 600 \Omega$$

$$\text{Capacitive reactance, } X_C = \frac{1}{\omega C} = \frac{1}{10000 \times 0.5 \times 10^{-6}} = 200 \Omega$$

$$\text{Impedance, } Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{300^2 + (600 - 200)^2} = \sqrt{300^2 + 400^2} = 500 \Omega$$

23. (a) $3.07 \times 10^{-8} \text{ H}$

Explanation: Frequency,

$$f = \frac{c}{\lambda} = \frac{3 \times 10^8}{360} = \frac{1}{12} \times 10^7 \text{ Hz}$$

Required inductance,

$$L = \frac{1}{4\pi^2 f^2 C} = \frac{1}{4\pi^2 \left(\frac{1}{12} \times 10^7\right)^2 \times 1.2 \times 10^{-6}}$$

$$= 3.07 \times 10^{-8} \text{ H}$$

24.

(c) decreases the current

Explanation: The coil of choke in a circuit decreases the current.

25. (a) 1508Ω

Explanation: $L = 3 \text{ H}$, $f = 80 \text{ Hz}$

$$\text{Inductive reactance, } X_L = \omega L = 2\pi f L = 2 \times 3.14 \times 80 \times 3 = 1508 \Omega$$

26.

(b) 5.0 ampere

$$\text{Explanation: } \eta = \frac{V_s I_s}{V_p I_p}$$

$$\therefore I_p = \frac{V_s I_s}{\eta V_p} = \frac{440 \times 2}{0.80 \times 220} = 5 \text{ A}$$

27.

(d) X is a capacitor and $X_C = R$

Explanation: X is a capacitor and $X_C = R$

28.

(c) 193 Hz

Explanation: $V = 45 \text{ volt}$

$$L = 9.5 \text{ mH}$$

$$i = 3.9 \text{ A}$$

$$f = ?$$

$$V = i X_L = i \times \omega L = i \times 2\pi f L$$

Frequency of the source,

$$f = \frac{V}{i \times 2\pi L} = \frac{45}{3.9 \times 2 \times 3.14 \times 9.5 \times 10^{-3}} = 0.193 \times 10^3 = 193 \text{ Hz}$$

29.

(b) 40Ω , 5.75 A

Explanation: $R = 40 \Omega$

$$L = 5 \text{ H}$$

$$C = 80 \mu F$$

$$\text{Impedance in series LCR circuit, } Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$\text{At resonance, } \omega L = \frac{1}{\omega C}$$

$$\text{Hence, } Z = \sqrt{R^2 + 0} = R = 40 \Omega$$

$$V = 230 \text{ Volt}$$

Hence current,

$$i = \frac{V}{Z} = \frac{230}{40} = 5.75 \text{ A}$$

30.

(c) inductor decreases and the capacitor increases.

Explanation: inductor decreases and the capacitor increases.

31. (b) 0.831
Explanation: $R = 300.0 \, \Omega$, $X_C = 300.0 \, \Omega$ and $X_L = 500.0 \, \Omega$
 $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{300^2 + (500 - 300)^2} = 100\sqrt{13} \, \text{ohm}$
 Now, power factor, $\cos \phi = \frac{R}{Z}$
 $\cos \phi = \frac{300}{100\sqrt{13}} = 0.831$
32. (a) 200 V - 50 Hz
Explanation: $\varepsilon_2 = \frac{N_2}{N_1} \cdot \varepsilon_1 = \frac{500}{50} \times 20 = 200 \, \text{V}$
 The frequency remains unchanged.
33. (a) 200 V - 50 Hz
Explanation: $\varepsilon_s = \frac{N_s}{N} \cdot \varepsilon_p$
 $= \frac{5000}{500} \times 20 = 200 \, \text{V}$
 frequency remains the same.
34. (c) Over a full cycle the capacitor C does not consume any energy from the voltage source.
Explanation: The current in a capacitor is ahead of voltage in phase by 90° .
 $P_{av} = \varepsilon_{ms} I_{rms} \cos\left(-\frac{\pi}{2}\right) = 0$
35. (d) R, L
Explanation: The phase difference between the alternating current and emf in R-L circuit varies between zero to $\frac{\pi}{2}$, but never equal to $\frac{\pi}{2}$.
36. (c) $[M^0 L^0 T A^0]$
Explanation: CR is the time constant of CR-circuit.
 $\therefore [CR] = [M^0 L^0 T A^0]$
37. (c) 0.79 W
Explanation: $X_L = \omega L = 314 \times 20 \times 10^{-3} = 6.28 \, \Omega$
 $X_C = \frac{1}{\omega C} = \frac{1}{314 \times 100 \times 10^{-6}} = 31.84 \, \Omega$
 $Z = \sqrt{R^2 + (X_C - X_L)^2}$
 $= \sqrt{50^2 + (31.84 - 628)^2} \, \Omega$
 $= \sqrt{2500 + (25.56)^2} \, \Omega$
 $= \sqrt{2500 + 635.3} \, \Omega$
 $= \sqrt{3153.3} \, \Omega$
 $P_{av} = \left(\frac{V_{rms}}{Z}\right)^2 R$
 $= \left(\frac{10}{\sqrt{2}}\right)^2 \times \frac{50}{3153.3} \, \text{W}$
 $= 0.79 \, \text{W}$
38. (c) Zero
Explanation: In pure AC capacitor Circuit, the current leads the voltage by an angle of 90 degrees.
 Power in Pure Capacitor Circuit Instantaneous power is given by $P = VI$
 $P = (V_m \sin \omega t)[I_m \sin(\omega t + \frac{\pi}{2})]$
 $\Rightarrow P = I_m V_m \sin \omega t \cos \omega t$
 $\Rightarrow P = \frac{I_m}{\sqrt{2}} \frac{V_m}{\sqrt{2}} \sin 2\omega t$
 So, $P_{avg} = 0$
 Hence, from the above equation, it is clear that the average power in the Capacitor circuit is zero.

39.

(c) Power

Explanation: Energy losses be zero in transformers hence power remains constant in step down and step up transformer also.

40.

(b) 127 μF

Explanation: Voltage and current will be in phase when $X_C = X_L$

$$\text{Or, } \frac{1}{\omega C} = \omega L$$

$$\text{Or, } \frac{1}{2\pi f C} = 2\pi f L$$

$$\text{Or, } C = \frac{1}{4\pi^2 f^2 L}$$

$$\text{Or, } C = \frac{1}{4 \times (3.14)^2 \times (50)^2 \times 80 \times 10^{-3}}$$

$$\therefore C = 127 \mu\text{F}$$

41.

(d) 400

Explanation: N_p = no. of turns in primary coil = 4000

N_s = no. of turns in secondary coil

V_p = input voltage = 2300 V

V_s = output voltage = 230 V

$$\text{Now, } \frac{V_s}{V_p} = \frac{N_s}{N_p}$$

$$\frac{230}{2300} = \frac{N_s}{4000}$$

Thus, $N_s = 400$

42.

(d) 0.064 H

$$\text{Explanation: } Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$L = (QR)^2 C$$

$$= (0.4 \times 2 \times 10^3)^2 \times 0.1 \times 10^{-6} \text{ H}$$

$$= 0.064 \text{ H}$$

43.

(c) $\text{ML}^2\text{T}^{-3}\text{I}^{-2}$

Explanation: Impedance has the same dimensions as the resistance.

$$[Z] = [R] = \frac{V}{I} = \frac{\text{ML}^2\text{T}^{-3}\text{I}^{-1}}{\text{I}^{-1}} = [\text{ML}^2\text{T}^{-3}\text{I}^{-2}]$$

44. (a) $\frac{10}{\sqrt{2}}$ V

Explanation: $V_R = V_L = V_C = 10\text{V}$

$$\Rightarrow R = X_L = X_C \text{ and } Z = R$$

$$V = IR = 10 \text{ V}$$

When the capacitance is short-circuited,

$$Z' = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + R^2} = \sqrt{2}R$$

$$\text{New current, } I' = \frac{V}{Z'} = \frac{V}{\sqrt{2}R} = \frac{10}{\sqrt{2}R}$$

$$V'_L = I' X_L = \frac{10}{\sqrt{2}R} \times R = \frac{10}{\sqrt{2}} \text{ V}$$


45. (a) $R / (R^2 + \omega^2 L^2)^{1/2}$

Explanation:

In an LR-circuit, e.m.f leads the current by phase angle ϕ , which is given by

$$\tan\phi = \frac{\omega L}{R}$$

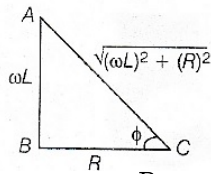Therefore, power factor, $\cos \phi = \frac{1}{\sqrt{1+\tan^2 \phi}}$



$$\Rightarrow \cos \phi = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{\sqrt{1 + (\omega L/R)^2}}$$

$$= \frac{1}{\sqrt{1 + \tan^2 \phi}} = \frac{1}{\sqrt{1 + (\omega L/R)^2}} = \frac{R}{\sqrt{R^2 + \omega^2 L^2}}$$

46.

(d) equal to natural frequency of LCR system

Explanation: For maximum current in LCR series circuit, impedance Z will be minimum. Now,

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Impedance Z will be minimum when $X_L = X_C$

Hence,

$$\omega L = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

This is equal to natural frequency of LCR system.

47.

(b) 220 V, 50 Hz

Explanation: In India, we use electricity at 220 volt and 50 hertz.

48.

(d) mutual induction

Explanation: A transformer works on the principle of mutual induction.

49. (a) soft iron

Explanation: Soft iron is used for the core of a transformer because of its high permeability and low hysteresis loss.

50.

(c) frequency

Explanation: Input and output voltages have same frequency in a transformer.

51.

(c) 90 %

Explanation: The efficiency of a transformer

$$\eta = \frac{\text{Output power}}{\text{Input power}} = \frac{V_s I_s}{V_p I_p}$$

Here $V_s I_s = 100 \text{ W}$, $V_p = 220 \text{ V}$, $I_p = 0.5 \text{ A}$

$$\therefore \eta = \frac{100}{220 \times 0.5} = 0.90 = 90 \%$$

52. (a) 7.61mA

Explanation: $R = 200\Omega$, $L = 0.4\text{H}$, $C = 5\mu\text{F} = 5 \times 10^{-6}\text{F}$, $\omega = 400\text{rad/s}$, $E = 3\text{volt}$

Now, $X_L = \omega L = 400 \times 0.4 = 160\Omega$

$$X_C = \frac{1}{\omega C} = \frac{1}{400 \times 5 \times 10^{-6}} = 500\Omega$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2} = \sqrt{200^2 + (500 - 160)^2} = 394.46\Omega$$

$$i = \frac{E}{Z} = \frac{3}{394.46} = 0.00761\text{A} = 7.61\text{mA}$$

53.

(c) eddy current

Explanation: Lamination increases the resistance and hence reduced the eddy current.

54.

(b) 80 Ω

Explanation: $V_R = 1.20 \cos(2500t)$

Thus, $\omega = 2500 \text{ rad/s}$

$$C = 5 \mu F = 5 \times 10^{-6} F$$

Capacitive reactance,

$$X_C = \frac{1}{\omega C} = \frac{1}{2500 \times 5 \times 10^{-6}} = 80 \Omega$$

55.

(c) 5.5 V

Explanation: $V_s = \frac{N_s}{N_p} \times V_p = \frac{100}{2000} \times 110 = 5.5 \text{ V}$

56.

(b) 0 W, 0 W

Explanation: $P = VI \cos \phi$

Average power consumed by inductor is zero as actual voltage leads the current by $\frac{\pi}{2}$ and $(\cos \frac{\pi}{2} = 0)$.

Average power consumed by capacitor is zero as actual voltage lags the current by $\frac{\pi}{2}$ and $(\cos \frac{\pi}{2} = 0)$.


57. (a) 10 Ω

Explanation: 10 Ω

58.

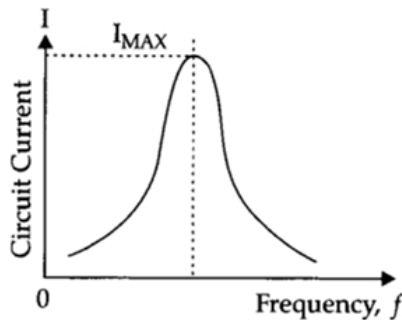(b) L, C and R

Explanation: The frequency vs. circuit current graph in a series LCR circuit is as follows, where current initially increases, reaches a maximum and then decreases with increase in frequency.



Hence, the circuit contains a combination of L, R and C.

59.

(b) 115.0 Ω

Explanation: $R = 115 \Omega$

$$C = 1.25 \mu F = 1.25 \times 10^{-6} F$$

$$L = 4.5 mH = 4.5 \times 10^{-3} H$$

Resonant angular frequency,

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4.5 \times 10^{-3} \times 1.25 \times 10^{-6}}} = \frac{1}{7.5 \times 10^{-5}}$$

Given that the angular frequency of the ac source $\omega = \omega_0$. It means that $X_L = X_C$

Hence, Impedance,

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{115^2 + 0}$$

$$Z = 115 \Omega$$

60. (a) Current

Explanation: Current increases in a step-down transformer.

61. (a) $\frac{\pi}{2}$

Explanation: $E = E_0 \sin \omega t$

$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right)$$

62.

(b) 13.3 μF

Explanation: $V = 170 \text{ volt}$, $f = 60 \text{ Hz}$, $i = 0.85 \text{ A}$

$$V = i X_C = i \frac{1}{\omega C} = \frac{i}{2\pi f C}$$

Thus, Capacitance required,

$$C = \frac{i}{2\pi f V} = \frac{0.85}{2 \times 3.14 \times 60 \times 170} = 13.3 \times 10^{-6} F = 13.3 \mu F$$

63. (a) $8 \times 10^5 \text{ Hz}$

Explanation: $f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$
 $= \frac{1}{2 \times 3.14} \sqrt{\frac{1}{250 \times 10^{-6} \times 0.16 \times 10^{-3}} - \frac{20 \times 20}{(0.16 \times 10^{-3})^2}}$
 $= 8 \times 10^5 \text{ Hz}$

64. (d) 0.05 J

Explanation: $U = \frac{1}{2} LI^2$
 $= \frac{1}{2} \times 100 \times 10^{-3} \times (1)^2 = 0.05 \text{ J}$

65. (c) $\omega = \frac{1}{LC}$

Explanation: At resonance,
 $X_L = X_C$
 $\omega L = \frac{1}{\omega C}$
 $\omega^2 = \frac{1}{LC}$
 $\omega = \frac{1}{\sqrt{LC}}$

66. (a) 90°

Explanation: 90°

67. (b) 25 V

Explanation: The resultant voltage in the LCR series circuit is calculated as,
 $V = \sqrt{V_R^2 + (V_C \sim V_L)^2}$
 Here, all alphabets are in their usual meanings.
 $V_R = 20 \text{ V}, V_C = 30 \text{ V and } V_L = 15 \text{ V}$
 So, $V = \sqrt{(20)^2 + (30 \sim 15)^2}$
 $V = \sqrt{400 + 225} = \sqrt{625}$
 $V = 25 \text{ V}$

68. (a) 90%

Explanation: $\eta = \frac{\text{output power}}{\text{input power}} = \frac{V_s I_s}{V_p I_p} \times 100 = \frac{100}{220 \times 0.5} \times 100 = 90\%$

69. (d) zero

Explanation: Here, the phase difference between current and e.m.f.,
 $\phi = \pi/2$
 $\therefore P_{av} = E_V I_V \cos \phi = E_V I_V \cos \pi/2 = 0$

70. (d) 50 amp

Explanation: $\frac{N_s}{N_p} = \frac{i_p}{i_s} = \frac{V_s}{V_p} = r$
 Given that $\frac{N_p}{N_s} = \frac{1}{25}$
 $i_s = 2 \text{ amp}$
 Thus, $\frac{25}{1} = \frac{i_p}{2}$
 $i_p = 50 \text{ amp}$

71. (d) $\sqrt{R^2 + (X_L - X_C)^2}$

Explanation: $\sqrt{R^2 + (X_L - X_C)^2}$

72. (a) 84.8 V

Explanation: $V_{\text{rms}} = 0.707 V_0 = 0.707 \times 120 \text{ V} = 84.8 \text{ V}$

73.

(d) $\frac{1}{4}$

Explanation: $\omega = \frac{1}{\sqrt{LC}}$

For, $\omega = \text{constant} \rightarrow \sqrt{LC} = \text{constant}$

Therefore, C is inversely proportional to L

So, if C is made 4C then L should be reduced to $\frac{L}{4}$ to keep ω constant.


74. (a) A.C. voltage

Explanation: A transformer changes the magnitude of a.c.

75.

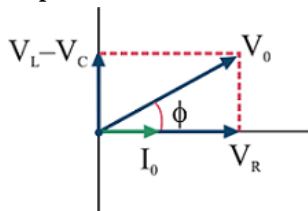(b) 76.7 V

Explanation: Consider RLC circuit phasor diagram:



Hence,

$$\cos \phi = \frac{V_R}{V_0}$$

$$\cos 31.5^\circ = \frac{V_R}{90}$$

$$\text{Thus, } V_R = 90 \times \cos 31.5^\circ = 90 \times 0.852 = 76.7 \text{ V}$$